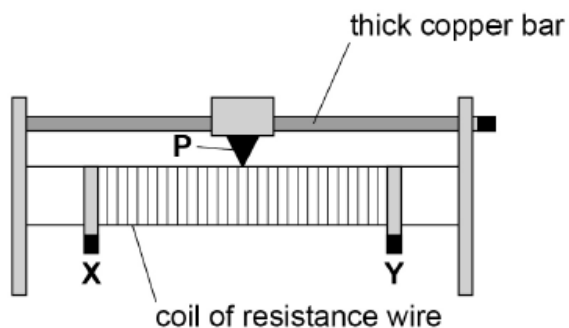


Electricity – 2022 AS Physics

1. June /2022/Paper_7407/1/No.8

0 8

Figure 11 shows a variable resistor that has a maximum resistance of 25Ω . A sliding contact **P** is mounted on a thick copper bar. **P** can be set to any position between **X** and **Y**.


Figure 11

0 8 . 1

Figure 12 shows the variable resistor being used to investigate the variation of current with voltage for a filament lamp.

The normal operating voltage of the lamp is 12 V .

The 12 V battery has negligible internal resistance.

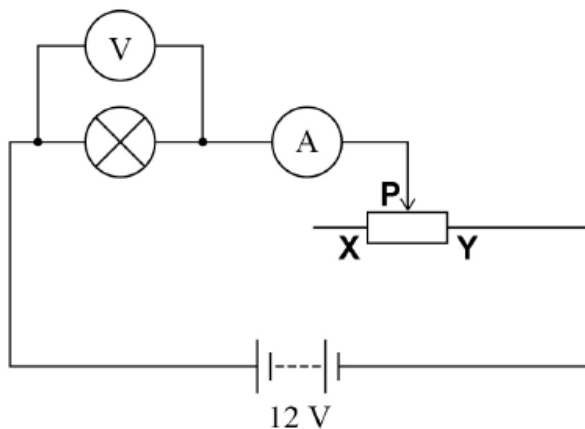Figure 12

The position of **P** is adjusted so that the reading on the voltmeter is at its minimum value of 0.75 V .

Calculate the resistance of the lamp when the voltmeter reading is 0.75 V .


[2 marks]

resistance = _____ Ω

0 8 . 2

Figure 13 shows the variation of current with voltage for the lamp between 2 V and 12 V.

Figure 13

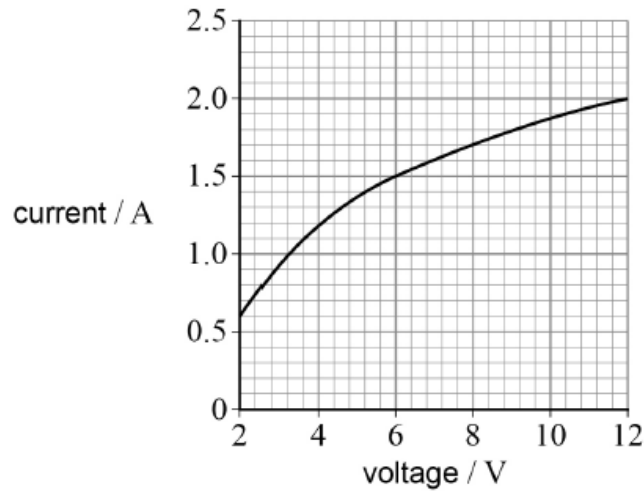

Calculate the resistance of the lamp when the voltage across the lamp is 8.0 V.

[2 marks]

resistance = _____ Ω

0 8 . 3


Explain, in terms of electron movement, why the resistance of the filament lamp changes as the voltage changes as shown in Figure 13.

[3 marks]

0 8 . 4

Figure 14 shows an alternative circuit used to investigate the variation of current with voltage for the lamp.

Figure 14

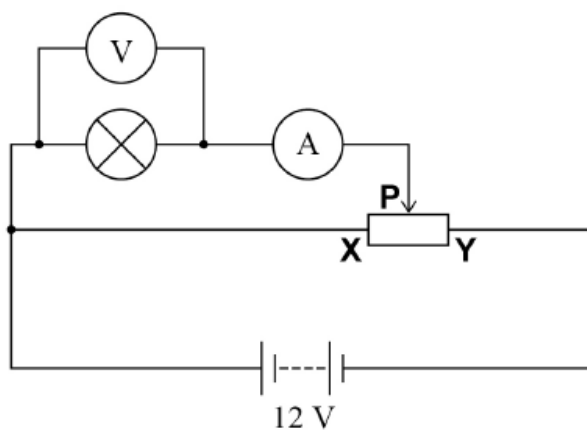

The circuit components are the same as in Figure 12.
When the voltage across the lamp is 12 V its resistance is 6.0Ω .

P is moved to position Y.

Calculate the total resistance of the circuit.

[2 marks]

total resistance = _____ Ω

0 8 . 5

Calculate the power transferred by the battery when P is at position Y.

[2 marks]


power = _____ W

2. June /2022/Paper_ 7407/2/No.2

0 2

Figure 3 shows a circuit used to find the resistance per unit length of a copper wire.

Figure 3


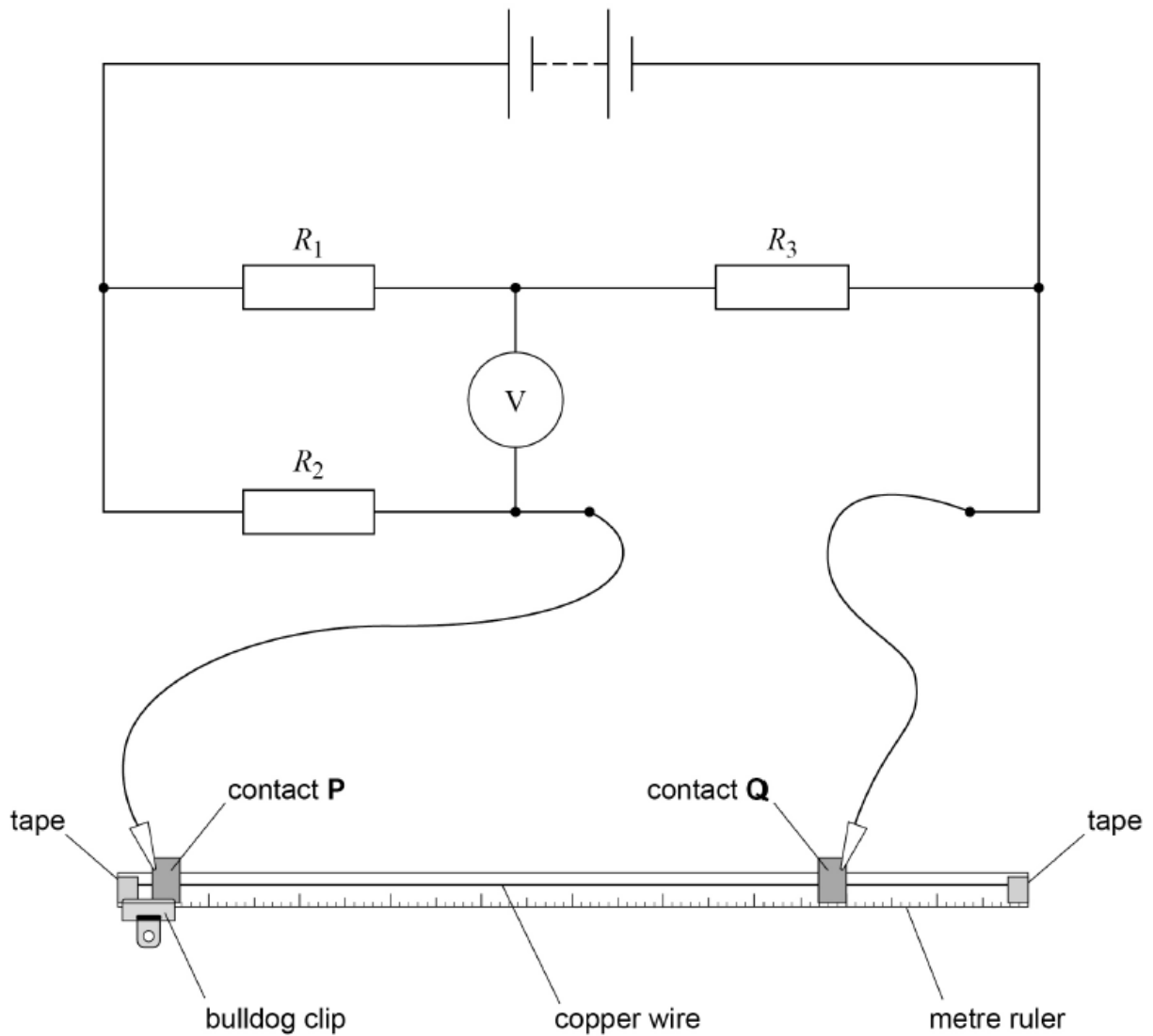


The copper wire is fixed with tape to a metre ruler that has 2 mm graduations. Contact P is placed on the wire close to one end of the ruler and held firmly in place using a bulldog clip. When contact Q is placed on the wire as shown in **Figure 3** the voltmeter shows a non-zero reading.

Q is moved along the wire until the voltmeter reading is zero.

Figure 4 shows enlarged views of the position of **P** and the new position of **Q**.

Figure 4

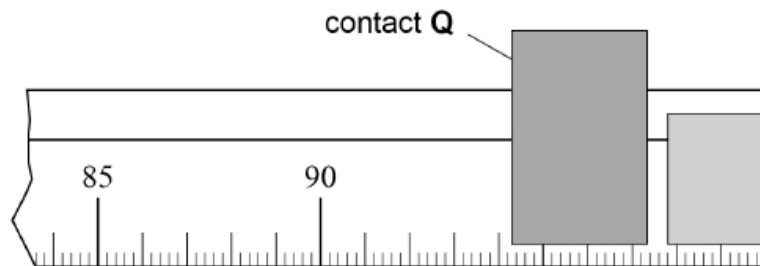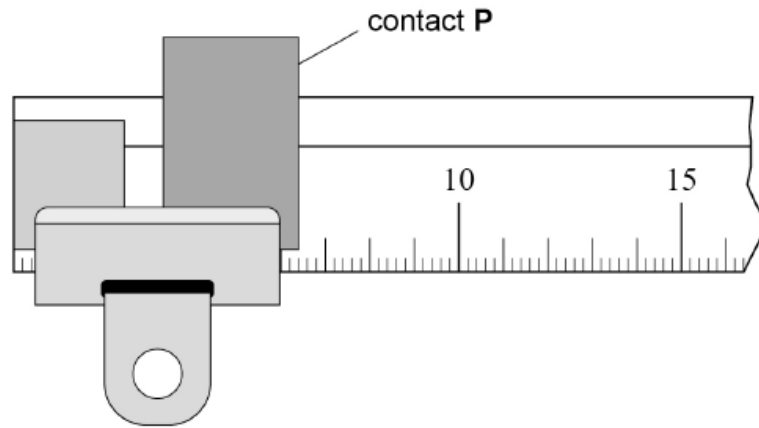

0 2 . 1

Determine, in m, the length x of copper wire between **P** and **Q**.

[1 mark]

$x =$ _____ m

0 2 . 2 When the voltmeter reading is zero:

$$\frac{R_1}{R_2} = \frac{R_3}{R_4}$$

where R_4 is the resistance of the copper wire between **P** and **Q**.

Determine, in $\Omega \text{ m}^{-1}$, the resistance per unit length of the copper wire.

$$R_1 = 2.2 \text{ M}\Omega$$

$$R_2 = 3.9 \text{ k}\Omega$$

$$R_3 = 75 \Omega$$

[2 marks]

resistance per unit length = _____ $\Omega \text{ m}^{-1}$

0 2 . 3 The diameter d of the copper wire is approximately 0.4 mm.

Suggest:

- a suitable measuring instrument to accurately determine d
- how to reduce the effect of random error on the result for d .

[3 marks]

0 2 . 4 Determine the resistivity ρ of copper.

diameter d of the copper wire = 0.38 mm

[2 marks]

$\rho =$ _____ $\Omega \text{ m}$

The copper wire is replaced with a constantan wire of diameter 0.38 mm.

$$\frac{\text{resistivity of constantan}}{\text{resistivity of copper}} = 30$$

0 2 . 5 Suggest **one** change to the circuit to make the voltmeter read zero for the same value of x as in Question 02.1.

[1 mark]


0 2 . 6 Calculate, in mm, the diameter of a constantan wire that has the **same** resistance per unit length as the copper wire.

[1 mark]

diameter = _____ mm

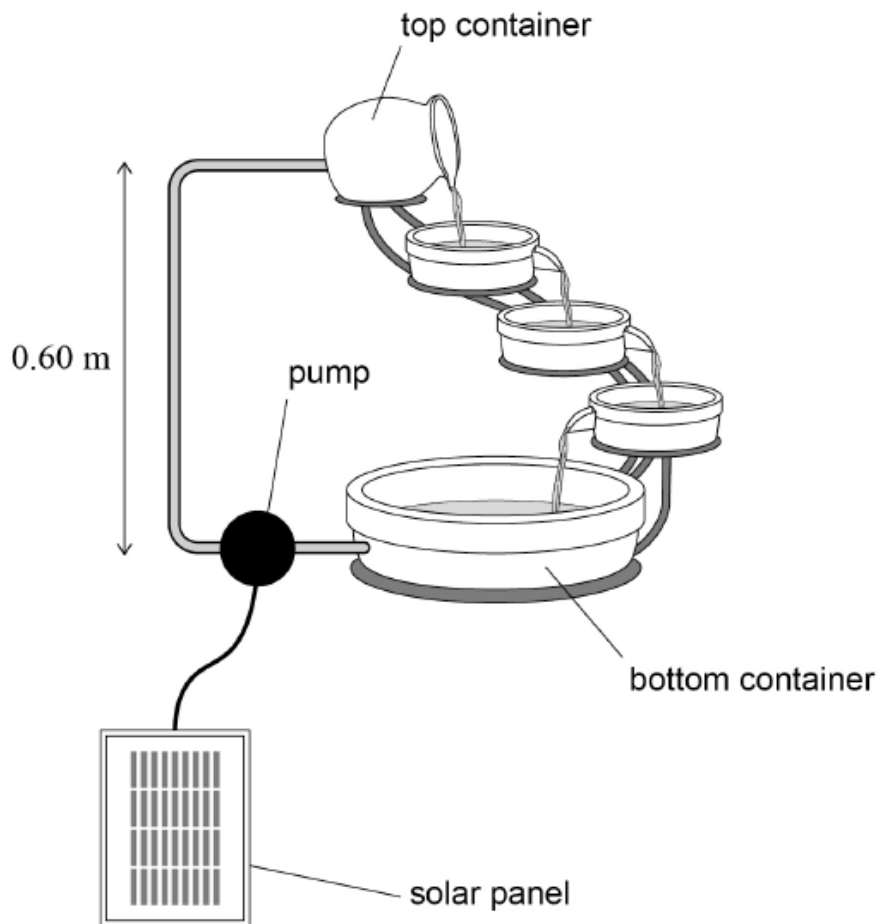3. June /2022/Paper_ 7407/2/No.28

A solar panel powers a pump for a water feature.



Solar energy is incident on the solar panel at a rate of 1.5 W.
Water from the bottom container is continually pumped through a vertical height of 0.60 m to the top container.

The overall efficiency of the solar panel and the pump is 20%.

What mass of water can be pumped into the top container each second?

[1 mark]

- A** 5 g
- B** 50 g
- C** 100 g
- D** 250 g

4. June /2022/Paper_ 7407/2/No.30

As the temperature of a copper wire increases, its resistance

[1 mark]

- A remains constant.
- B increases.
- C decreases.
- D remains constant at first and then decreases.

5. June /2022/Paper_ 7407/2/No.31

A $12\ \Omega$ resistor is connected across the terminals of a cell that has an emf of $2.0\ \text{V}$ and an internal resistance of $4.0\ \Omega$.


What is the terminal pd?

[1 mark]

- A $0.50\ \text{V}$
- B $0.75\ \text{V}$
- C $1.30\ \text{V}$
- D $1.50\ \text{V}$

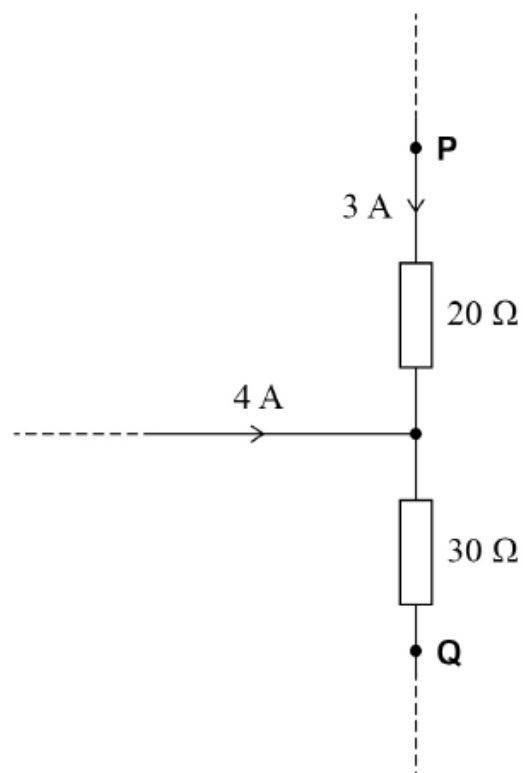6. June /2022/Paper_ 7407/2/No.32

The diagram shows the currents in part of a circuit.



What is the potential difference between points P and Q?

[1 mark]

A 60 V


B 70 V

C 180 V

D 270 V

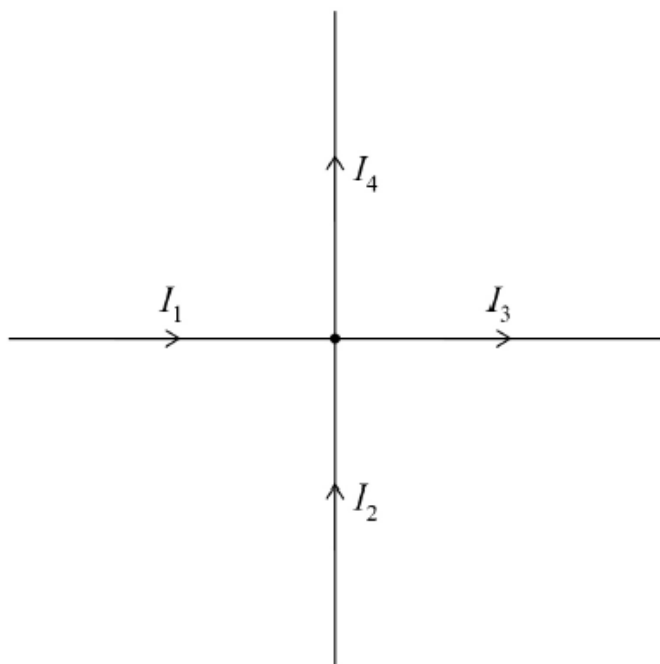7. June /2022/Paper_ 7407/2/No.33

The currents in the four wires obey the relationship $I_1 + I_2 + I_3 + I_4 = 0$



This relationship is an expression of the law of conservation of

[1 mark]

A charge.

B energy.

C potential difference.

D power.

8. June /2022/Paper_ 7407/2/No.34

A practical power supply provides a steady current I for a time t to an external circuit.

The emf of the power supply during t is equivalent to

[1 mark]

- A** the energy dissipated in the external circuit.
- B** the energy dissipated in the whole circuit.
- C** the energy dissipated in the whole circuit, divided by the product It .
- D** the potential difference across the terminals of the power supply.