

Electricity – AS Physics

1. No.6


0 6 . 1

State what is meant by the emf (electromotive force) of a battery.

[1 mark]

The amount of chemical energy transferred to electrical energy for 1 C of charge through the battery

Figure 10 shows the circuit diagram for a battery-powered torch. The circuit contains three identical light emitting diodes (LEDs) and a resistor **R**. The current in the circuit is 44 mA .

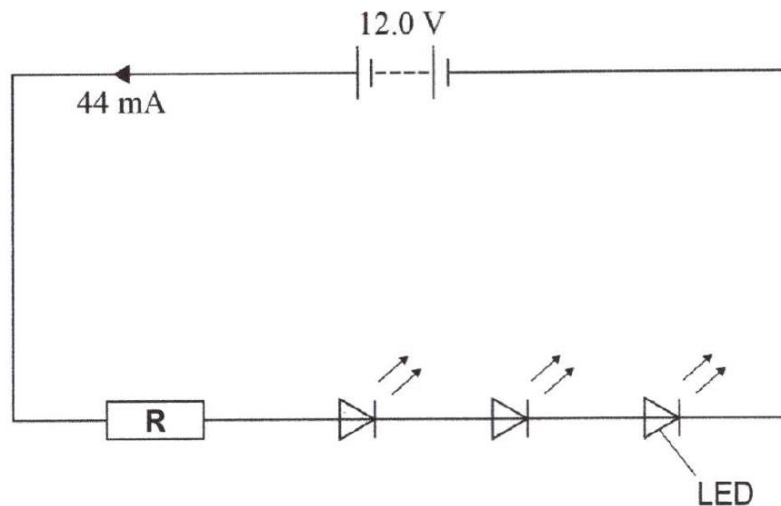Figure 10

0 6 . 2

Calculate the number of electrons that pass a point in the circuit in 37 minutes.

[2 marks]

$$Q = It \quad \text{and} \quad Q = ne \Rightarrow n = \frac{Q}{e}$$

$$Q = 0.044 \times 37 \times 60$$

$$Q = 97.68\text{ C}$$


So

$$n = \frac{97.68}{1.6 \times 10^{-19}} = 6.1 \times 10^{20}$$

number of electrons = 6.1×10^{20}

Figure 11 is the current–voltage characteristic for an LED used in the torch.

Figure 11

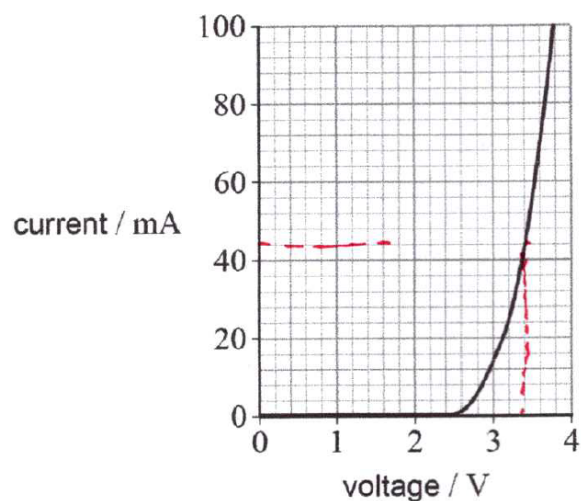

0 6 . 3 Determine the power output of one LED when the torch is on.

[3 marks]

$$\text{when } V \approx 3.4 \text{ V}, I = 44 \text{ mA}$$

$$P = VI$$

$$= 3.4 \times 44 \times 10^{-3}$$

$$= 0.1496 \text{ W}$$

power output = 0.15 W

The battery has an emf of 12.0 V and an internal resistance of 1.5 Ω .

0 6 . 4 Determine the resistance of R in Figure 10.

[4 marks]

$$\begin{aligned} \text{Lost volts} &= Ir \\ &= 0.044 \times 1.5 \\ &= 0.066 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{P.d} &= 12 - 0.066 \\ &= 11.934 \text{ V} \end{aligned}$$

$$\text{LED} \Rightarrow R = \frac{3.4}{0.044} = 77 \Omega$$

$$\begin{aligned} \text{In series, } R_T &= 3 \times 77 \\ &= 231 \Omega \end{aligned}$$

Total R of the circuit

$$R_T = \frac{12}{0.044} = 273 \Omega$$


$$\begin{aligned} &= 273 - 231 - 1.5 \\ &= 40.5 \Omega \end{aligned}$$

resistance = 40.5 Ω

0 6 . 5 Another appliance is connected to the battery as shown in **Figure 12**.

The current in the battery is 3.5 A when switch **S** is closed.

Figure 12

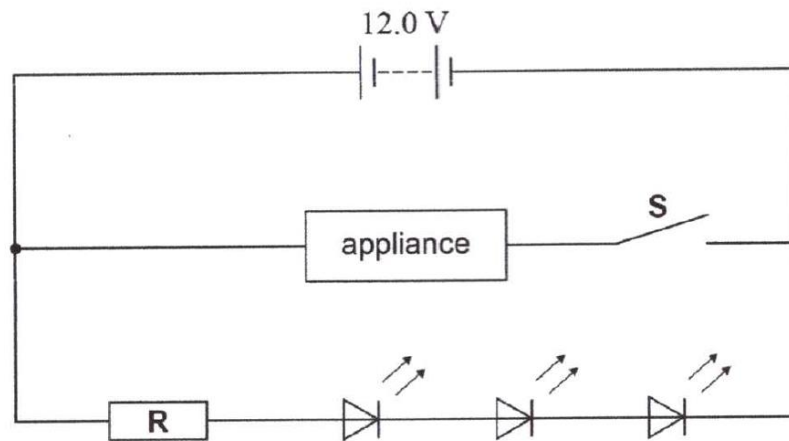

Each LED requires a voltage of at least 2.9 V to light.

Deduce whether the LEDs will light when **S** is closed.


[3 marks]

When $V = 2.9\text{ V}$, $I = 8\text{ mA}$ so 3 LED, $P_d = 3 \times 2.9$
 $= 8.7\text{ V}$ to light
 Terminal $P_d = 6.75\text{ V}$, so LED won't
 light as $8.7\text{ V} > 6.75\text{ V}$.

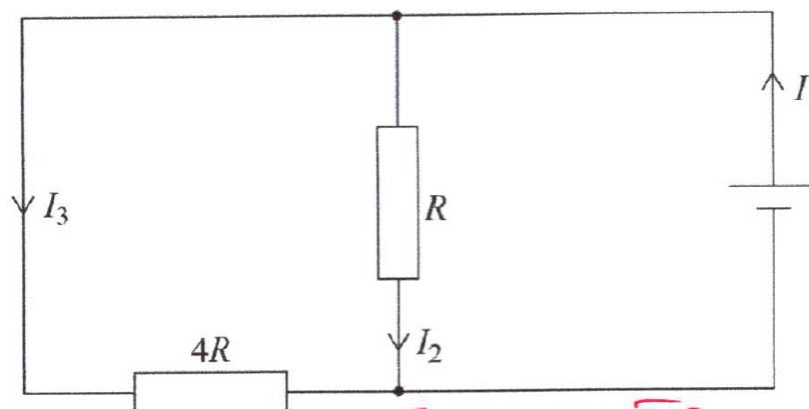2. June/2023/Paper_7407/2/No.11

A cell with negligible internal resistance is connected to two resistors of resistance $4R$ and R .

The currents I_1 , I_2 and I_3 in the circuit are shown.



Same $V = IR$

Which equation is correct for this circuit?

$$I = \frac{V}{R}$$

[1 mark]

A $I_1 = 4I_2$

☐

B $I_1 = 4I_3$

☐

C $I_2 = 4I_3$

☒

D $I_3 = 4I_1$

☐

So
 $I \propto \frac{1}{R} \times 4$
 $\div 4$


So
 $I_3 = \frac{I_2}{4}$

or

$$4I_3 = I_2$$

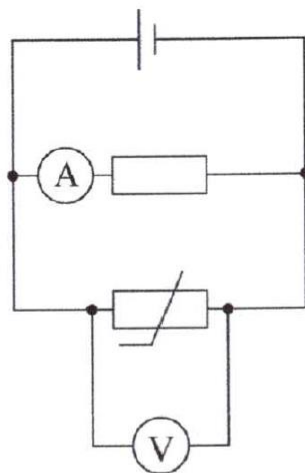3. June/2023/Paper_7407/2/No.18

A circuit contains a thermistor and a resistor in parallel. The internal resistance of the cell is negligible.



*Temp ↑ so R ↓
and V is unchanged
and so I is
unchanged for
resistor*

The temperature of the thermistor is increased.
The temperature of the resistor is kept constant.

What is observed on the voltmeter and the ammeter?

[1 mark]

	Voltmeter reading	Ammeter reading	
A	decreases	increases	☐
B	increases	increases	☐
C	no change	increases	☐
D	no change	no change	☒

4. June/2023/Paper_7407/2/No.19

The table shows the lengths and cross-sectional areas of two wires **X** and **Y** of the same metal.

Wire	Length / cm	Cross-sectional area / mm ²
X	47	0.10
Y	23	0.40

The resistance of **X** is 6.0 Ω .

The temperature of **Y** is the same as the temperature of **X**.

What is the resistance of **Y**?

$$R = \rho \frac{L}{A} \quad \text{so } R \propto \frac{L}{A}$$

[1 mark]

A 0.12 Ω

☐

B 0.73 Ω

☒

C 1.2 Ω

☐

D 3.1 Ω

☐

$$\frac{R_x A_x}{L_x} = \frac{R_y A_y}{L_y}$$

so

$$R_y = \frac{R_x \times A_x \times L_y}{A_y \times L_x}$$

$$= 6 \times \frac{1}{4} \times \frac{23}{47}$$





$$= 0.73$$

5. June/2023/Paper_7407/2/No.20

A superconducting material has a critical temperature T_c .

Which graph shows the variation of resistivity ρ with temperature T ?


[1 mark]

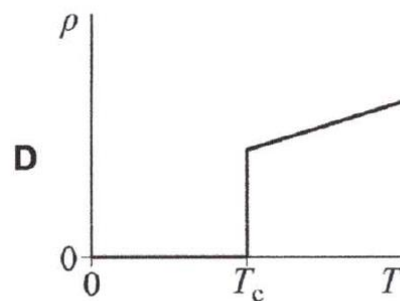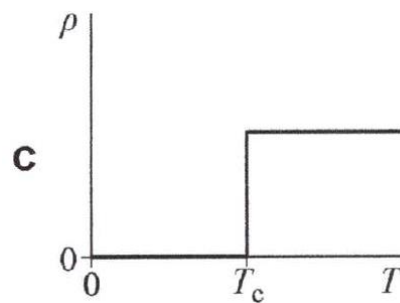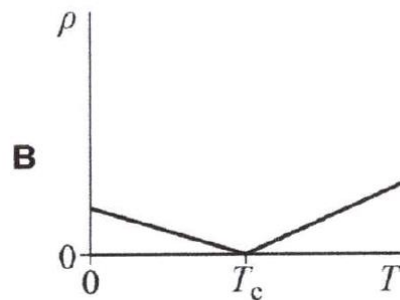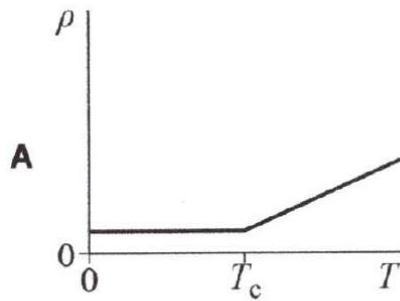

The resistivity decreases as Temperature decreases and as Temperature goes higher, it collapses and increases.

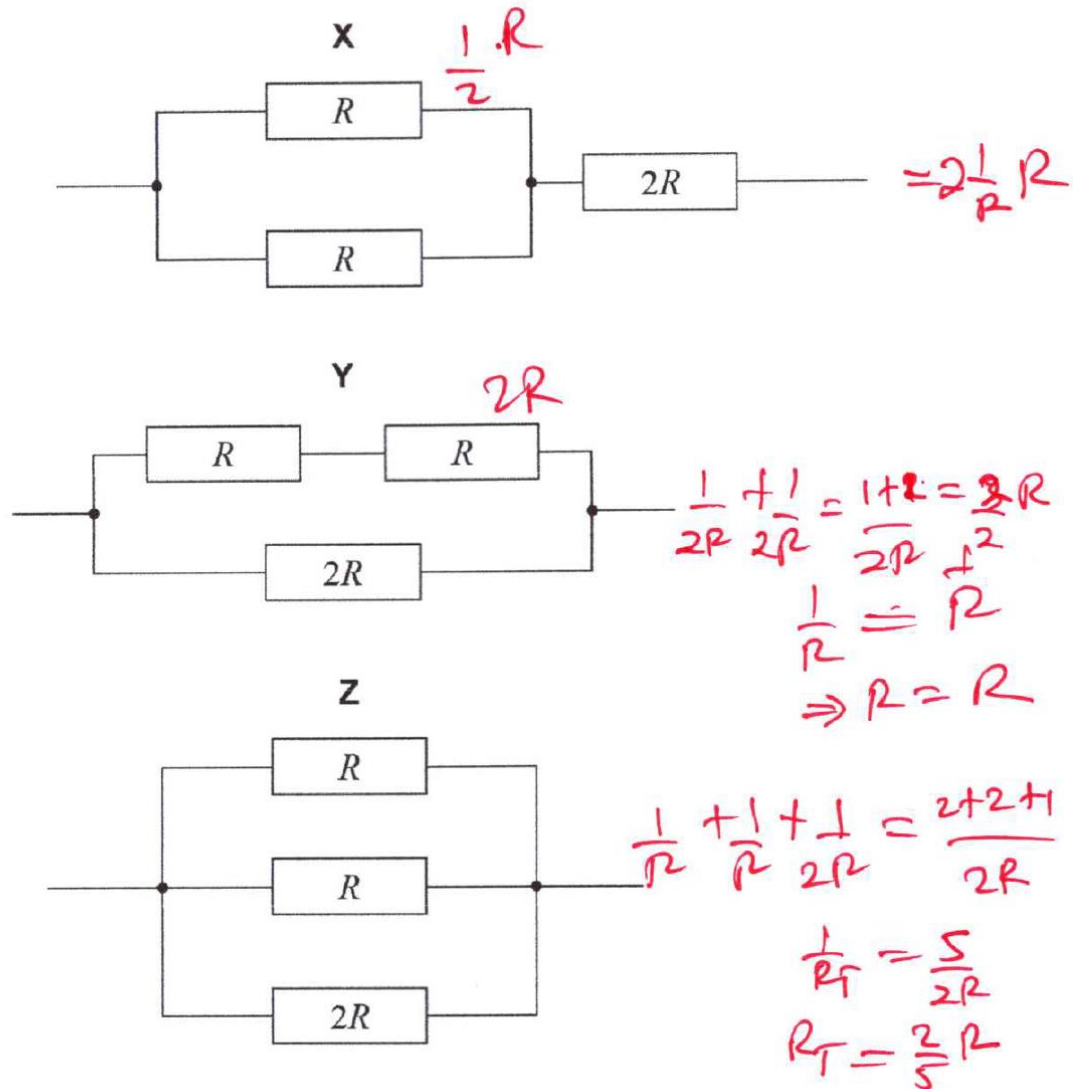6. June/2023/Paper_7407/2/No.21

X, Y and Z are three networks of resistors.



Which gives the networks in order of largest total resistance to smallest total resistance?

[1 mark]

A X, Y, Z



B Y, X, Z



C Z, X, Y



D Z, Y, X




7. June/2023/Paper_7407/2/No.28

Which row shows the resistance of an ideal ammeter and of an ideal voltmeter?

[1 mark]

	Resistance of ammeter	Resistance of voltmeter
A	zero	zero
B	zero	infinite
C	infinite	zero
D	infinite	infinite

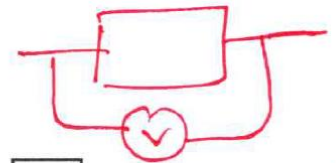

We need
no current
through it
so no
resistance
in
ammeter
and
infinite
resistance in
voltmeter

The current in a resistor is 15 mA.

How many electrons pass through the resistor in 3 minutes?

8. June/2023/Paper_7407/2/No.29

The current in a resistor is 15 mA.

How many electrons pass through the resistor in 3 minutes?

[1 mark]

A 2.8×10^{17}



B 1.7×10^{19}



C 2.8×10^{20}



D 1.7×10^{22}



Resistance in
voltmeter

$$I = 0.015$$

$$Q = It$$

$$= 0.015 \times 3 \times 60$$


$$= 1.6 \times 10^{-19}$$

$$= 1.7 \times 10^{19} \text{ electrons}$$

$$n = \frac{Q}{e}$$

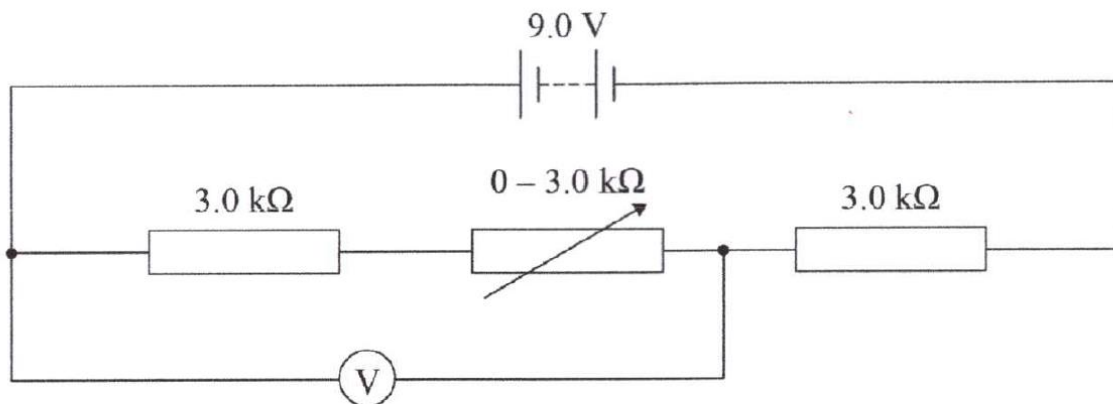9. June/2023/Paper_7407/2/No.30

Three resistors are connected in series with a 9.0 V battery of negligible internal resistance.



The resistance of the variable resistor is varied from 0 to 3.0 kΩ.

The range of potential difference observed on the voltmeter is

[1 mark]

A 0 to 6.0 V

☐

B 3.0 V to 6.0 V

☐

C 4.5 V to 6.0 V

☒

D 4.5 V to 9.0 V

☐


when 0, $V = 4.5\text{ V}$
when $3\text{ k}\Omega$, $V = 6\text{ V}$

10. June/2023/Paper_7407/2/No.31




The current–voltage characteristic between 0 and 6.0 V is required for a filament lamp. The lamp is connected in a circuit with a battery of emf 6.0 V and negligible internal resistance.

Which circuit should be used?

[1 mark]

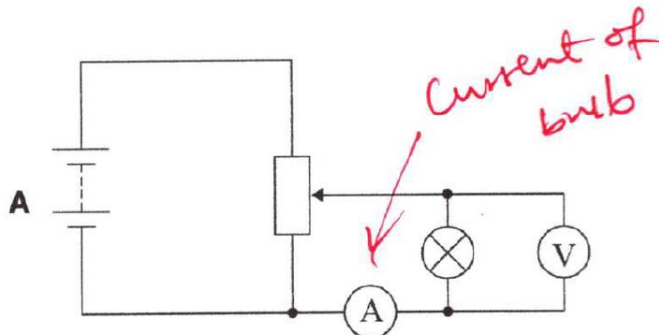

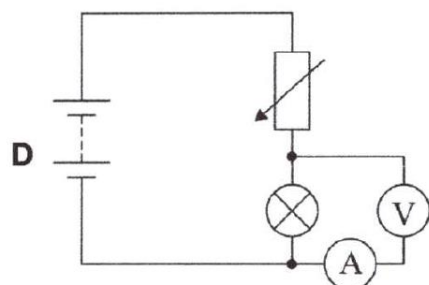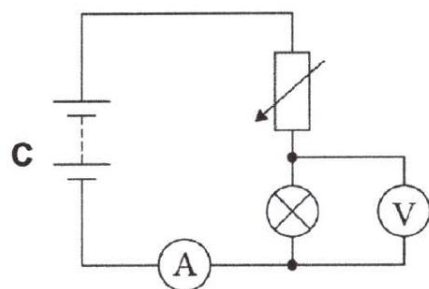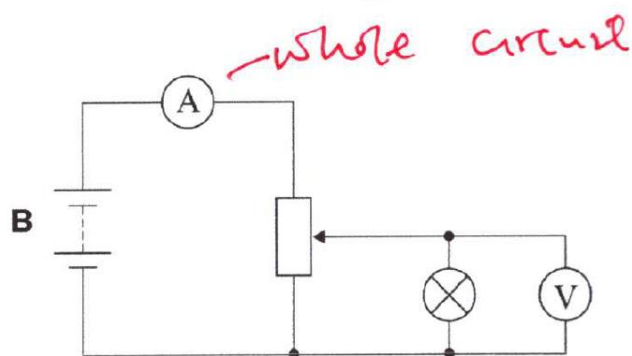
we can't have anything in series, so no C and D.



↑ can't be in parallel

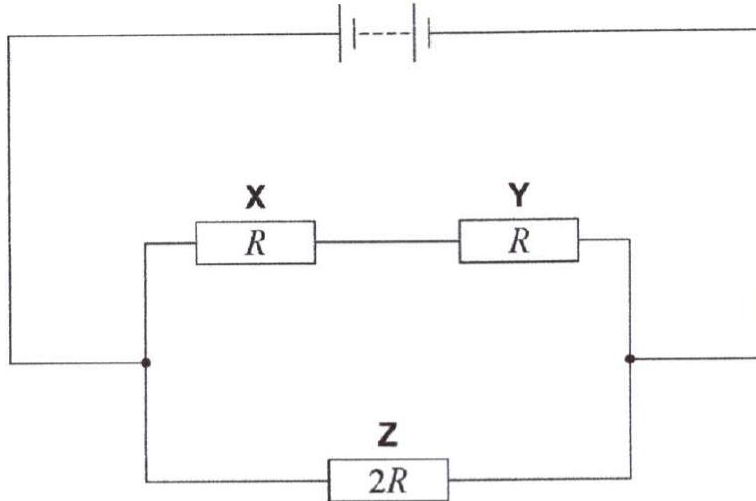11. June/2023/Paper_7407/2/No.32

The diagram shows a circuit containing three resistors X, Y and Z.



X and Y each have resistance R .
Z has resistance $2R$.

What is $\frac{\text{power in X}}{\text{power in Z}}$?

A $\frac{1}{4}$
☐
B $\frac{1}{2}$
☒

C 2

☐

D 4

☐

$$P = \frac{V^2}{R} = I^2 R = IV$$

$$\frac{P_X}{P_Y} = \frac{\frac{V_X^2}{R}}{\frac{V_Y^2}{2R}} = \frac{V_X^2}{V_Y^2} \times \frac{2R}{R} \quad [1 \text{ mark}]$$

$$\frac{P_X}{P_Y} = 2 \times \left(\frac{V_X^2}{V_Y^2} \right)$$

$$\frac{P_X}{P_Y} = \left(\frac{1}{2} \right)^2 \times 2 = \frac{1}{2}$$