

Electricity – GCSE CS Physics

1. No.4

0 4





A gardener wanted to build an electrical circuit to monitor the temperature in a greenhouse.

0 4 . 1

Which symbol represents an electrical component with a resistance that decreases as its temperature increases?

[1 mark]

Tick (✓) **one** box.

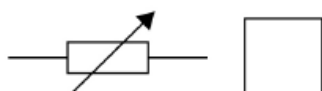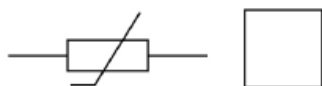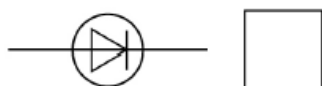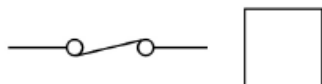

0 4 . 2

When the resistance of an electrical circuit decreases, the current in the circuit increases.

Complete the sentence.

Choose the answer from the box.

[1 mark]

charge	energy	potential difference	power
--------	--------	----------------------	-------


Electrical current is a flow of _____.

0 4 . 3

The gardener wanted to find how the resistance of the component varies with temperature.

Figure 4 shows the equipment used by the gardener.

Figure 4

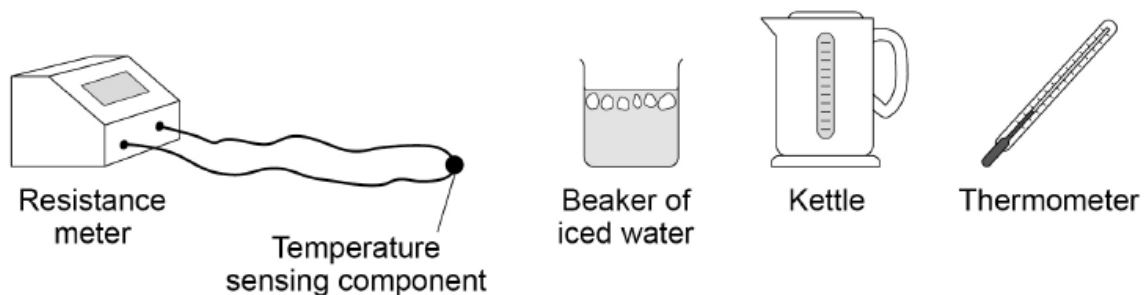


The resistance meter displays the resistance of the component.

Plan a method the gardener could use to find how the resistance of the component varies with temperature.

[4 marks]

Figure 5 shows how the resistance of the component varies with temperature.

Figure 5

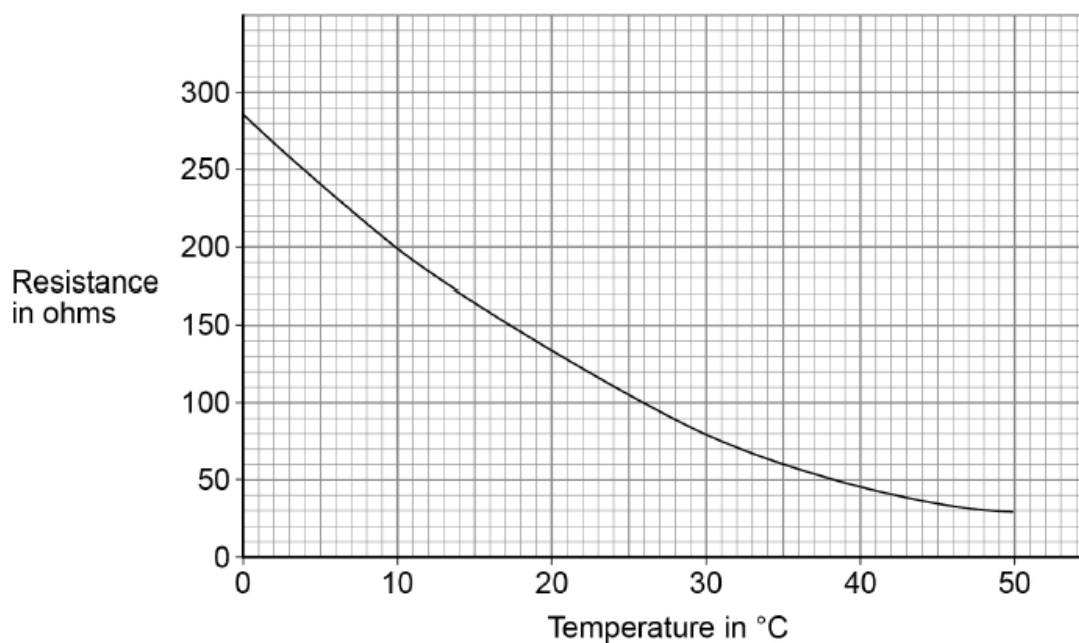

0 4 . 4 Complete the sentence.

Choose the answer from the box.

[1 mark]

linear

non-linear

directly proportional

The relationship between the temperature and the resistance of the component is _____.

04.5

The temperature in the greenhouse changed from 10°C to 30°C .

Determine the change in resistance of the component between these temperatures.

Use Figure 5.

[2 marks]

Change in resistance = _____ Ω

The gardener builds a circuit that switches a heater on when the greenhouse gets too cold.

Use the Physics Equations Sheet to answer questions 04.6 and 04.7.

04.6

Write down the equation that links current (I), potential difference (V) and power (P).

[1 mark]

04.7

The power of the heater is 2900 W .

The potential difference across the heater is 230 V .

Calculate the current in the heater.

[3 marks]

Current = _____ A

2. No.6

0 6

Body analysis scales use the electrical resistance of a person's legs to estimate the percentage of water in the person's body.

Figure 8 shows body analysis scales.

Figure 8




The person's legs contain both solid tissue and water.

A student used resistors to model the solid tissue and water.

The student connected a $20\ \Omega$ resistor in parallel with a resistor, R .

Figure 9 shows the circuit diagram.

Figure 9

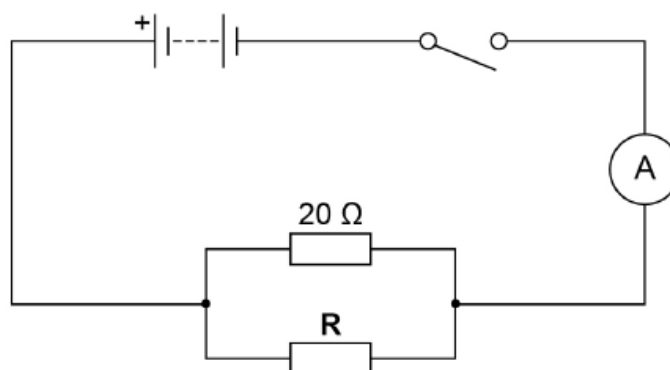

0 6 . 1

To determine the total resistance of both resistors, a voltmeter must be connected into the circuit.

Complete Figure 9 to show where the voltmeter should be connected.

[1 mark]

06.2

The student calculated the total resistance of the two resistors.

The student's answer was $26\ \Omega$.

Explain why the student's answer **cannot** be correct.

[2 marks]

Use the Physics Equations Sheet to answer questions 06.3 and 06.4.

06.3

Write down the equation that links current (I), resistance (R) and potential difference (V).

[1 mark]

06.4

When the total resistance of the resistors was $7.5\ \Omega$ the current in the circuit was $480\ \text{mA}$.

Calculate the potential difference across the two resistors.

[3 marks]

Potential difference = _____ V


The student investigated how the resistance of **R** affected the total resistance of the circuit.

Table 2 shows the results.

Table 2

Resistance of R in ohms	Total resistance of the circuit in ohms
5.0	4.0
10.0	6.7
15.0	8.6
20.0	10.0
25.0	11.1

Figure 10

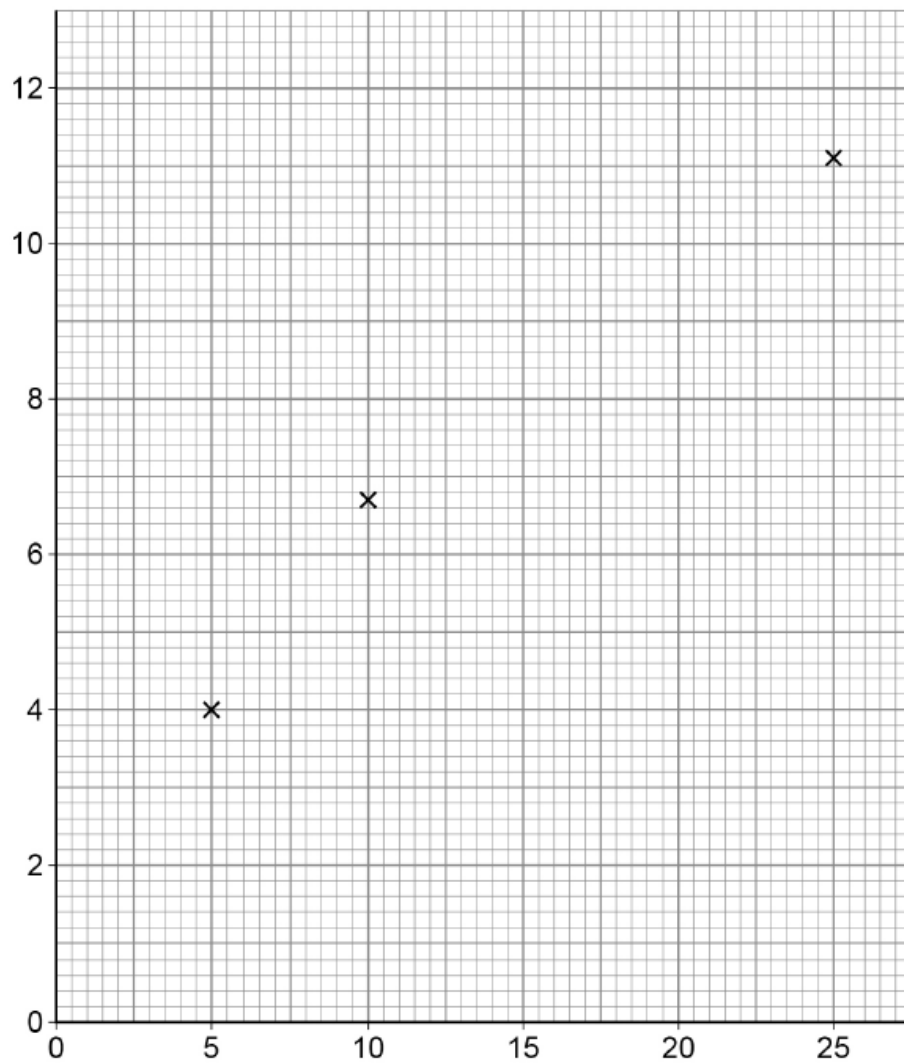

0 6 . 5 Complete Figure 10.

You should:

- label both axes
- plot the two remaining values from Table 2
- draw the line of best fit.

[3 marks]

0 6 . 6 What resistance of R would give a total resistance of 4.4Ω ?

Use Figure 10.

[1 mark]

Resistance of R = _____ Ω

The body analysis scales initially show a reading of 0.0 kg.

When the student steps onto the scales the reading is 64.8 kg.

The student steps off the scales and then immediately steps back on.

The scales now show a reading of 64.1 kg.

0 6 . 7 Complete the sentence.

[1 mark]


The difference between the two values given by the scales is due to a _____ error.

0 6 . 8 The height of the student is programmed into the scales.

The scales place the student into a category, **A**, **B** or **C**, based on height and mass.

Figure 11 shows how the scales use the category and the total resistance of the legs to determine the body water percentage.

Figure 11

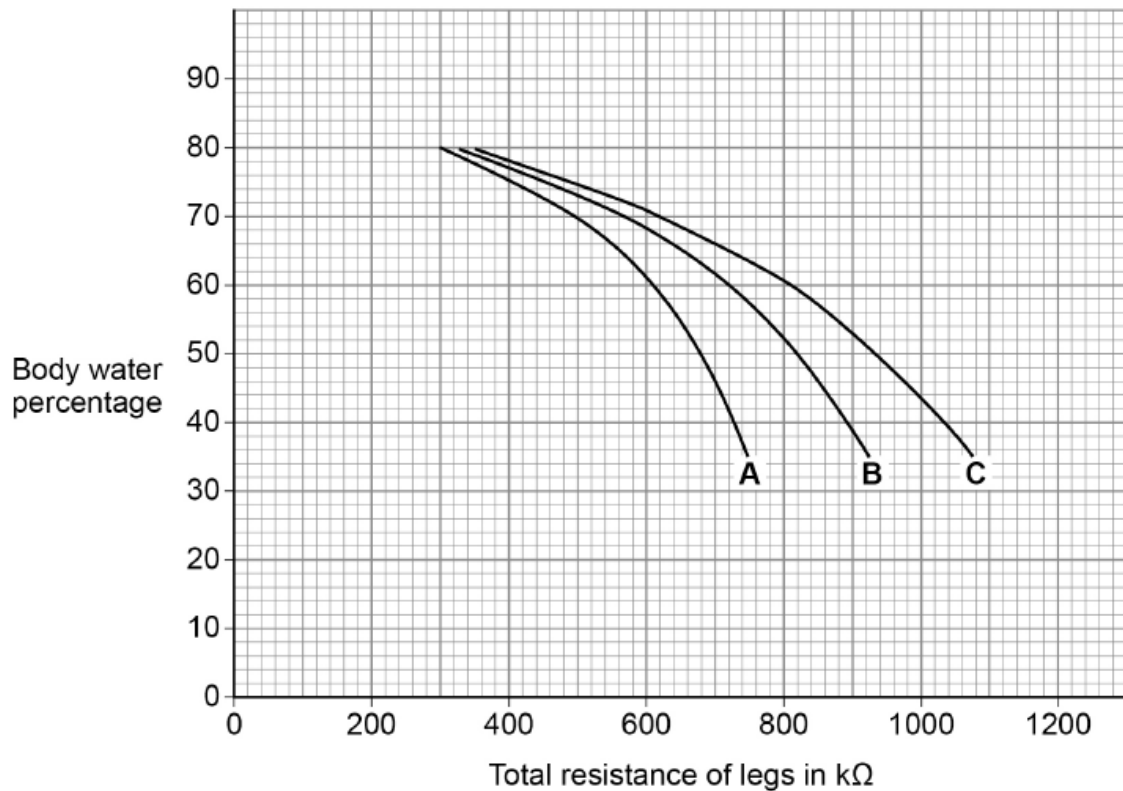

The total resistance of the student's legs is $600\text{ k}\Omega$. A healthy body water percentage is between 45% and 65%.

The different measurements of the mass of the student mean that the student could be in either category **A** or category **B**.


Evaluate if the student has a healthy body water percentage.

[3 marks]

3. No.3

0 3

Figure 7 shows how the National Grid transfers energy from a power station to some street lamps.

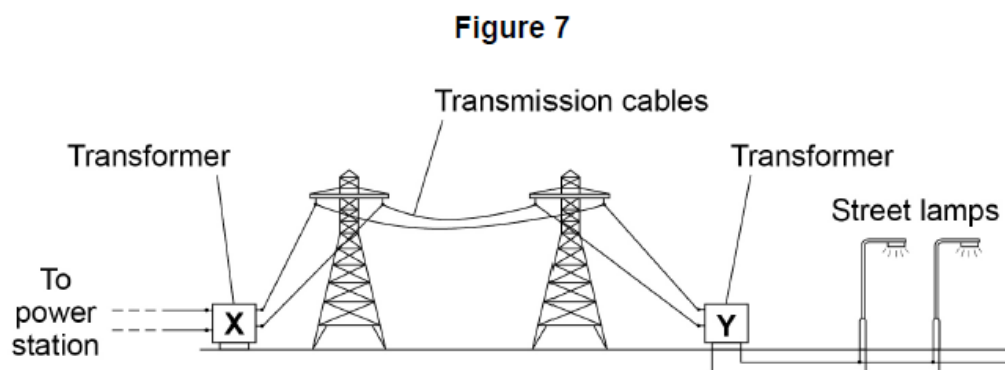

0 3 . 1

Explain how transformer X increases the efficiency of the National Grid.

[3 marks]

0 3 . 2

The potential difference across the primary coil in transformer Y is 400 000 V.

The potential difference across the secondary coil is 11 000 V.

The current in the primary coil is 660 A.

Calculate the current in the secondary coil of transformer Y.

Use the Physics Equations Sheet.

[3 marks]

Current in the secondary coil = _____ A

0 3 . 3

Why is the current in each street lamp less than the current in the secondary coil in transformer Y?

[1 mark]

Tick (✓) **one** box.

Current is used up in the cables between Y and each street lamp.

☐

Some of the current is dissipated to the surroundings.

☐


The cables between Y and the street lamps have electrical resistance.

☐

The street lamps are connected in parallel.


☐

0 3 . 4

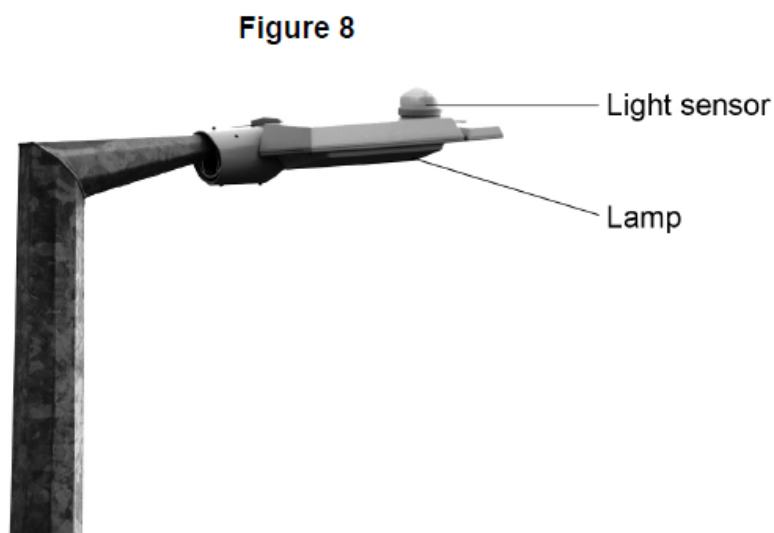Figure 8 shows the top of a street lamp.

The light sensor detects if it is day or night.

Figure 9 shows part of the circuit in the light sensor.

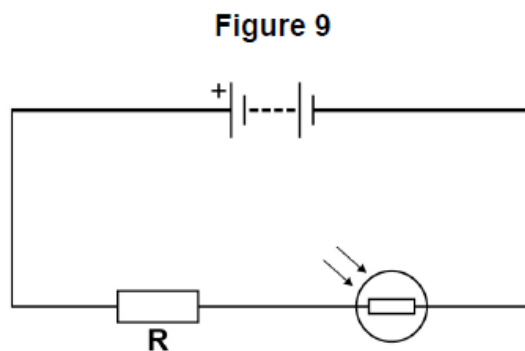

Explain what happens to the potential difference across resistor **R** as the light intensity decreases.

[3 marks]

0 3 . 5

When the current in resistor **R** is 20 mA, the power transferred by resistor **R** is 6.0 W.

Calculate the resistance of resistor **R**.

Use the Physics Equations Sheet.

[4 marks]

Resistance = _____ Ω